

# Verilog Lab 2



# Data Types for Signals or Variables

- **Wire type:** physical connections between ports  
(most popular type of input/internal signals)
  - wire  
wire reset, clock;  
wire [7:0] address;
- **Register types:** abstract data storage elements  
(only these types of signals can be on the **left-hand side of assignments in procedural blocks**)
  - reg: unsigned, varying width (most popular type of input/internal signals)  
reg carry\_out;  
reg [31:0] data\_a, data\_b;



# Example

~~wire out ;~~

reg out ;

always @(sel or in1 or in2) begin

if (sel == 1'b1) begin

out = in1;

end else begin

out = in2;

end

end



# Combinational vs Sequential Circuits

## Sequential circuits

- contain **memory** elements and logic gates
- the outputs are a function of the current inputs and the state of the memory elements.

## Combinational circuits

- consist of logic gates
- the outputs at any time are determined from **only the present** combination of inputs.




# Two types of always blocks
 
## Sequential block

- is triggered by **clock** and other signals.

```
always @(posedge clk or negedge rst_n) begin
    if (rst_n == 1'b1) begin
        q <= 0;
    end else begin
        q <= d;
    end
end
```



# Two types of always blocks

## ❓ Combinational block

- is triggered by the signals in the sensitivity list

Traditional style: full sensitivity list of the always block

```
always @(sel or in1 or in2) begin
```

```
    if (sel == 1'b1) begin
```

```
        out = in1;
```

```
    end else begin
```

```
        out = in2;
```

```
    end
```

```
end
```

Modern coding style:

```
always @* begin
```

You may also use combinational assignment. eg. assign out =(sel)?in1:in2;

# Procedural Assignment

## ❓ **Blocking** procedural assignment: =


- An assignment is completed before the next assignment starts.
- (assume a = 0)  
a = 1;  
c = a; // c = 1

## ❓ **Non-blocking** procedural assignment: <=

- Assignments are executed in parallel.
- (assume a = 0)  
a <= 1;  
c <= a; // c = 0



# Procedural Assignment

 


- ❑ Do not mix blocking and non-blocking in the same always block.
- ❑ Sequential circuits usually use non-blocking.
- ❑ Combinational circuits usually use blocking.
- ❑ Use blocking assignment for assign.






# Moore / Mealy machine

 
 
## Moore Outputs

Outputs depend solely on state vector (generally, a Moore FSM is the simplest to design)




## Mealy Outputs

Outputs depend on inputs and state vector (only use if it is significantly smaller or faster)

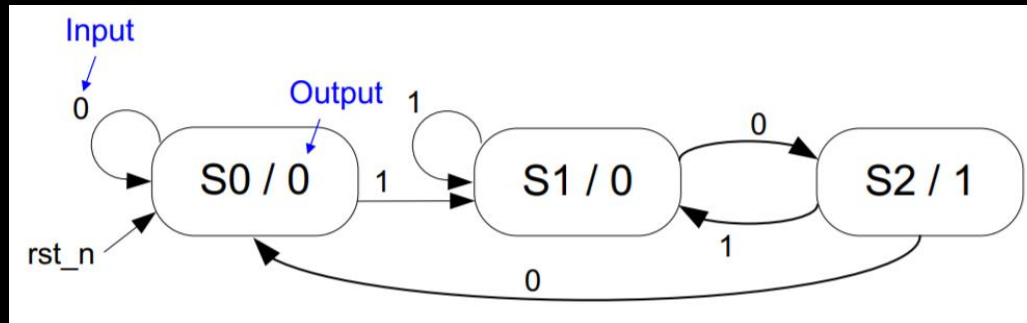
# Moore Machine Example

- Recognizing the “10” sequence among the input bit stream


 
# Mealy Machine Example

- Recognizing the “10” sequence among the input bit stream




# FSM design guideline

- ❑ An always block for updating state registers
  - Sequential block
- ❑ An always block for next state evaluation (state transition)
  - Combinational block
- ❑ Optional always blocks for output generation
  - Combinational block
- ❑ Parameterize all state encoding


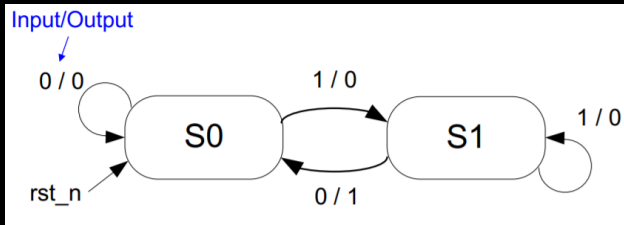
# Mealy Machine Example

```
parameter S0 = 1'b0;
parameter S1 = 1'b1;
reg state, next_state;
always @(posedge clk, negedge rst_n)
begin
    if (rst_n == 1'b0)
        state = S0;
    else
        state = next_state;
end
```



```
always @* begin
    next_state = S0;
    case(state)
        S0: begin
            if (in == 1)
                next_state = S1;
            else
                next_state = S0;
            end
        S1: begin
            if (in == 0)
                next_state = S0;
            else
                next_state = S1;
            end
        endcase // case end
    end // always end
    assign out = (state == S1 && in == 0) ? 1 : 0;
```



# Assignment 2



# Outline

- Function Description
- Framework Introduction in Block Diagram
- Testbench template
- nWave
- Precautions and Timeline



# GCD Engine

- Calculate the greatest common divisor (GCD) of two 8-bit positive integers
- Using a **START** signal to load inputs
- Generate a **DONE** signal when the calculation is finished
- Assert an **ERROR** signal when invalid inputs are detected





# GCD Engine

- The IO specification is shown below, and modification is unavailable:

```
module GCD (  
    input wire CLK,  
    input wire RST_N,  
    input wire [7:0] A,  
    input wire [7:0] B,  
    input wire START,  
    output reg [7:0] Y,  
    output reg DONE,  
    output reg ERROR  
);
```



# GCD Engine

- Inputs:
  - CLK: clock
  - RST\_N: reset (low active)
  - A, B: two 8-bit input numbers
  - START: indicate the valid input with one-cycle pulse
- Outputs:
  - Y: the answer
  - DONE: indicate the valid output with one-cycle pulse
  - ERROR: 0 means valid result while 1 means invalid one  
(invalid: either A or B is 0 at the start)



# Outline

- Function Description
- Framework Introduction in Block Diagram
- Testbench template
- nWave
- Precautions and Timeline




# GCD Engine


- Sequential circuits can be partitioned into **datapath** and **control unit**
  - ▣ Datapath: perform data processing, data registering, and data moving
  - ▣ Control unit: behavior control, state(mode) switching




# GCD Engine

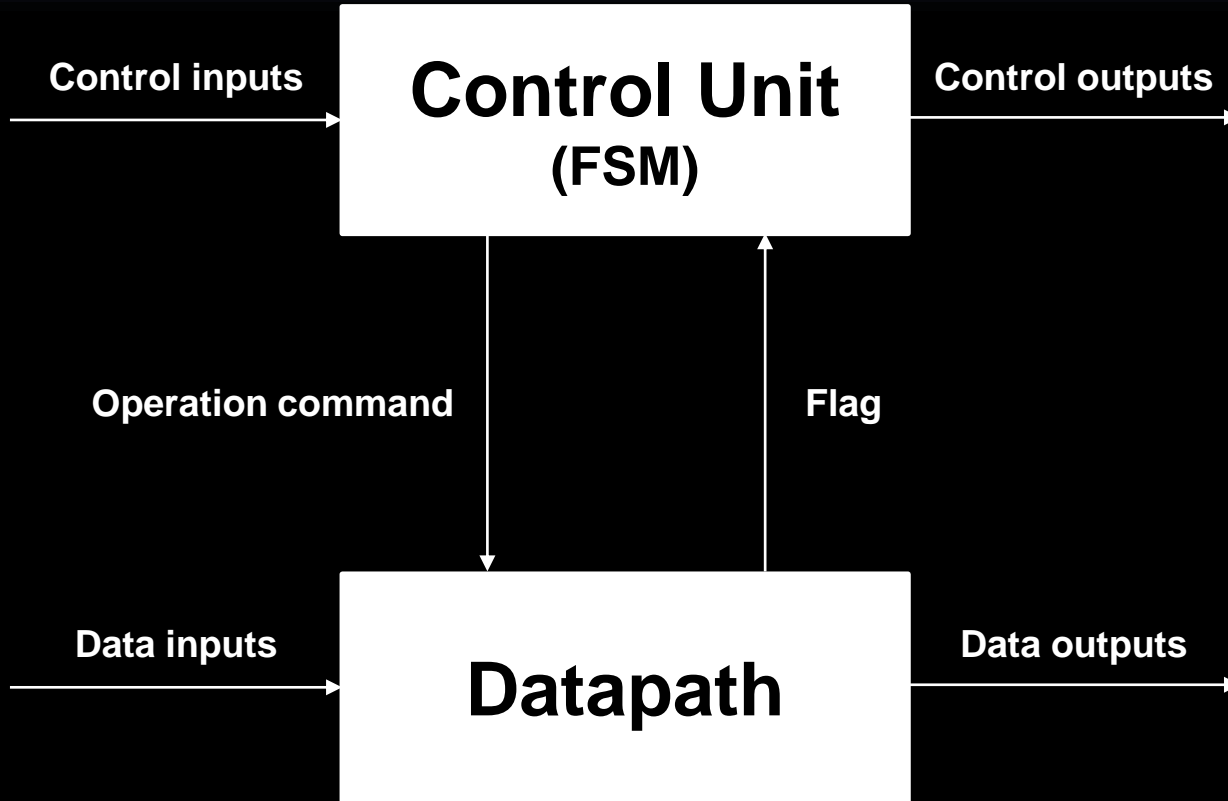

# GCD Engine

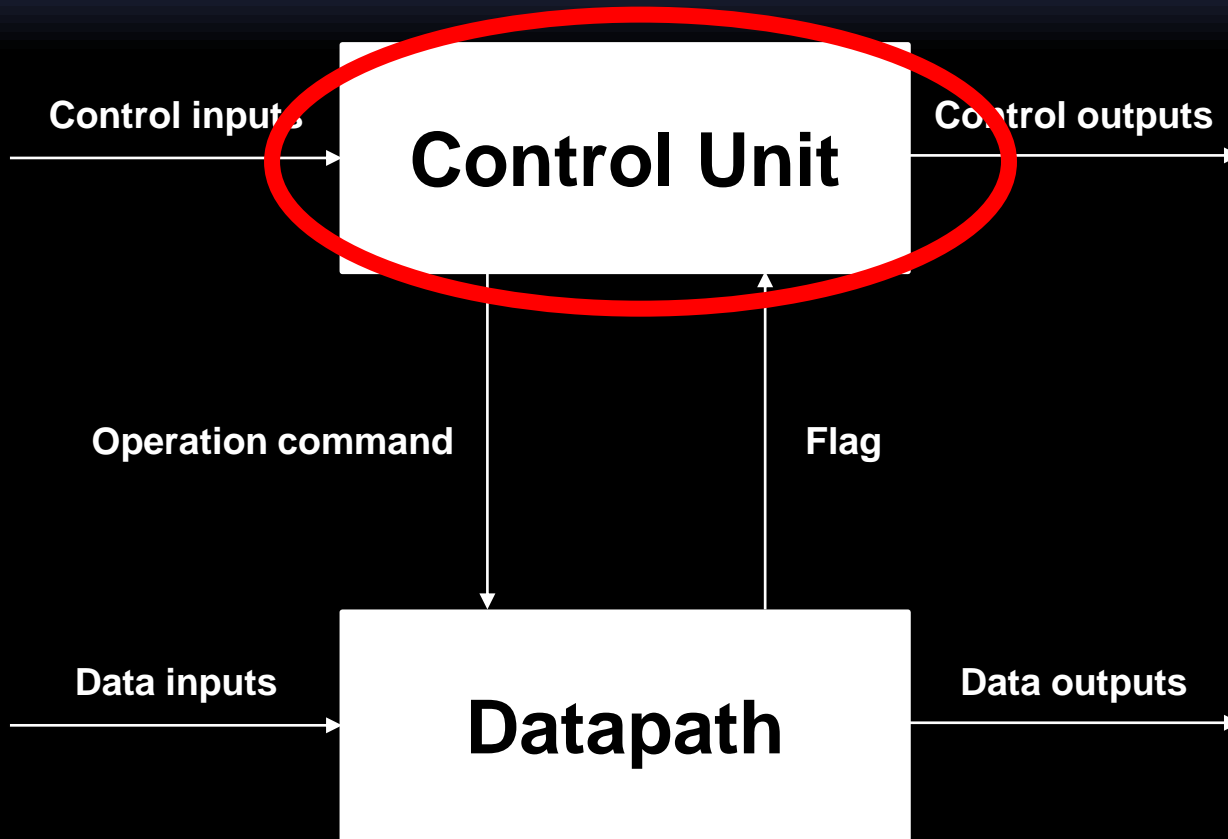

# GCD Engine

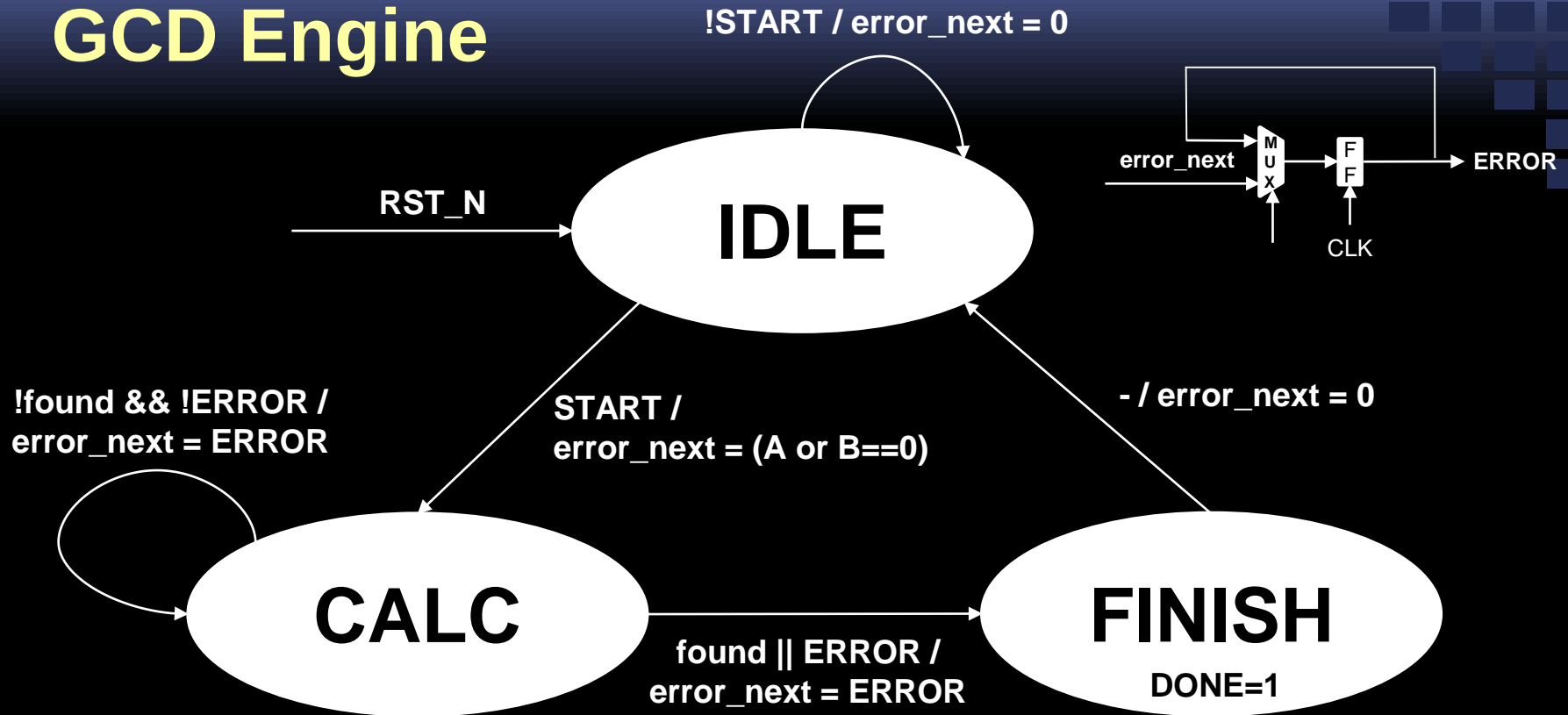

# GCD Engine


- Your design “must” include these components:

```
parameter [1:0] IDLE = 2'b00;  
parameter [1:0] CALC = 2'b01;  
parameter [1:0] FINISH = 2'b10;
```






# GCD Engine

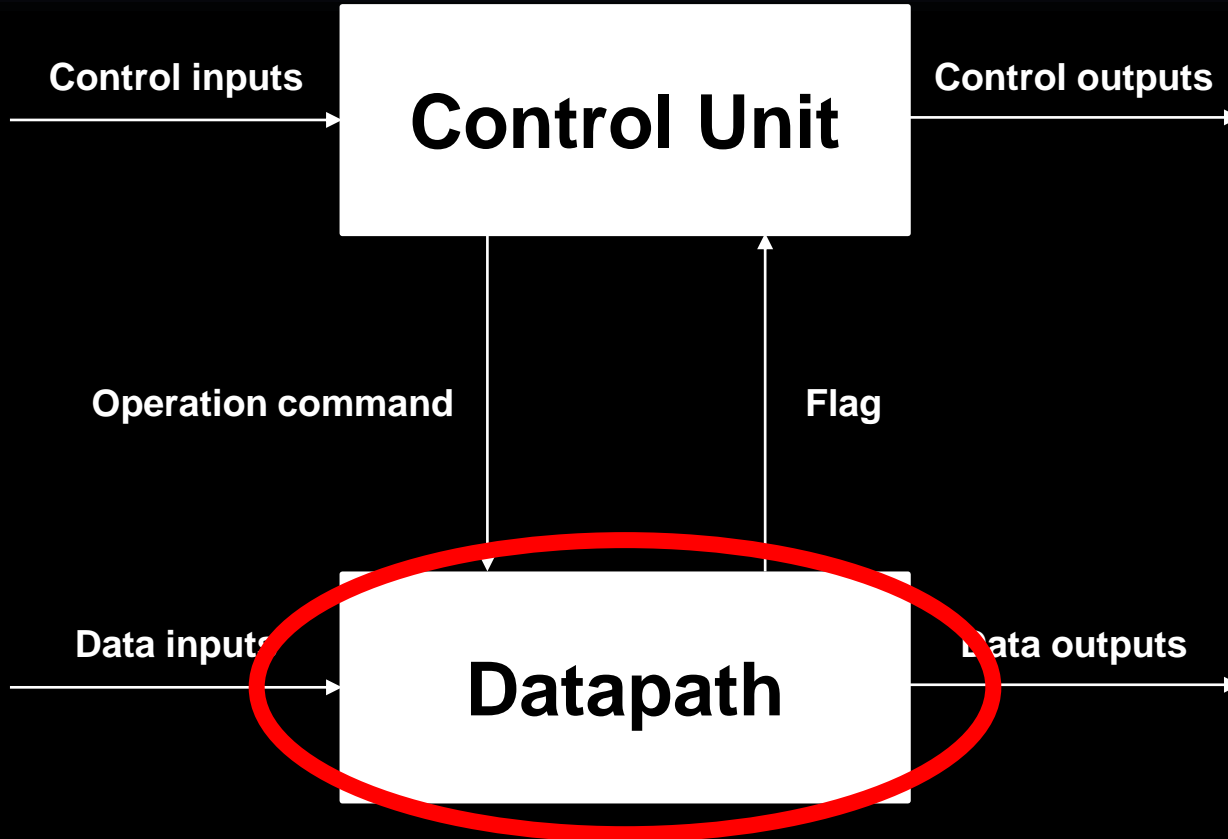

# GCD Engine

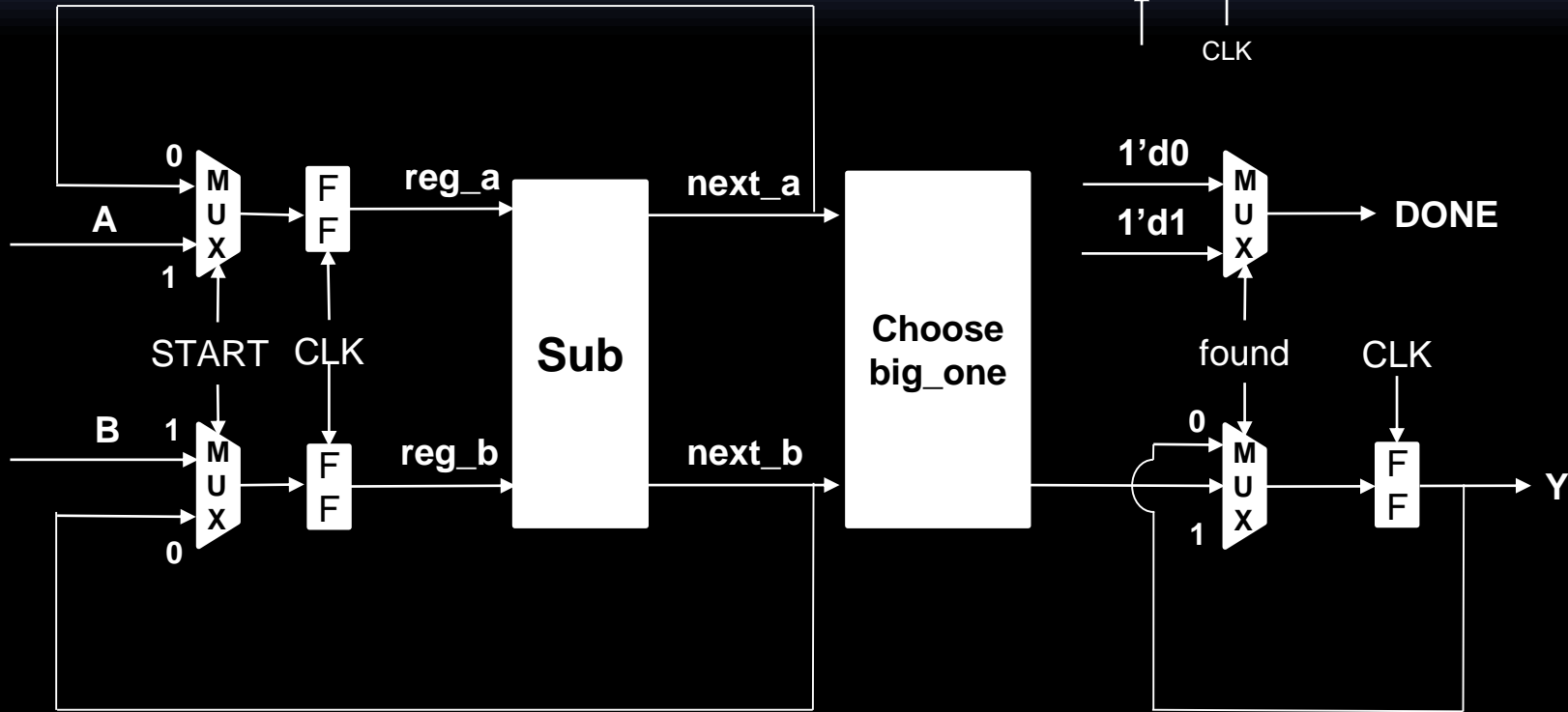

Warning: This is just a simplified version for easy understanding, the practical implementation can be more complicated.

# Example

- $(40,12) \rightarrow (28,12) \rightarrow (16,12) \rightarrow (4,12) \rightarrow (4,8) \rightarrow (4,4) \rightarrow (4,0)$
- 4 is the answer

`assign found =(next_a==0 ||next_b==0)?1:0;`

# GCD Engine

- Your design “must” include these components:

```
wire found, err
reg [7:0] reg_a, reg_b, next_a, next_b;
reg [7:0] big_one;
reg error_next;
reg [1:0] state, state_next;
```



# Outline

- Function Description
- Framework Introduction in Block Diagram
- Testbench template
- nWave
- Precautions and Timeline



# Testbench

- We will provide testbench file for this lab. You don't need to write it on your own.
- However, you can add your own cases on top of our test cases.
- Testbench file contains 5 basic cases. You will get 60% if you passed all 5 cases.




# Outline

- Function Description
- Framework Introduction in Block Diagram
- Testbench template
- nWave
- Precautions and Timeline




# Timing diagram

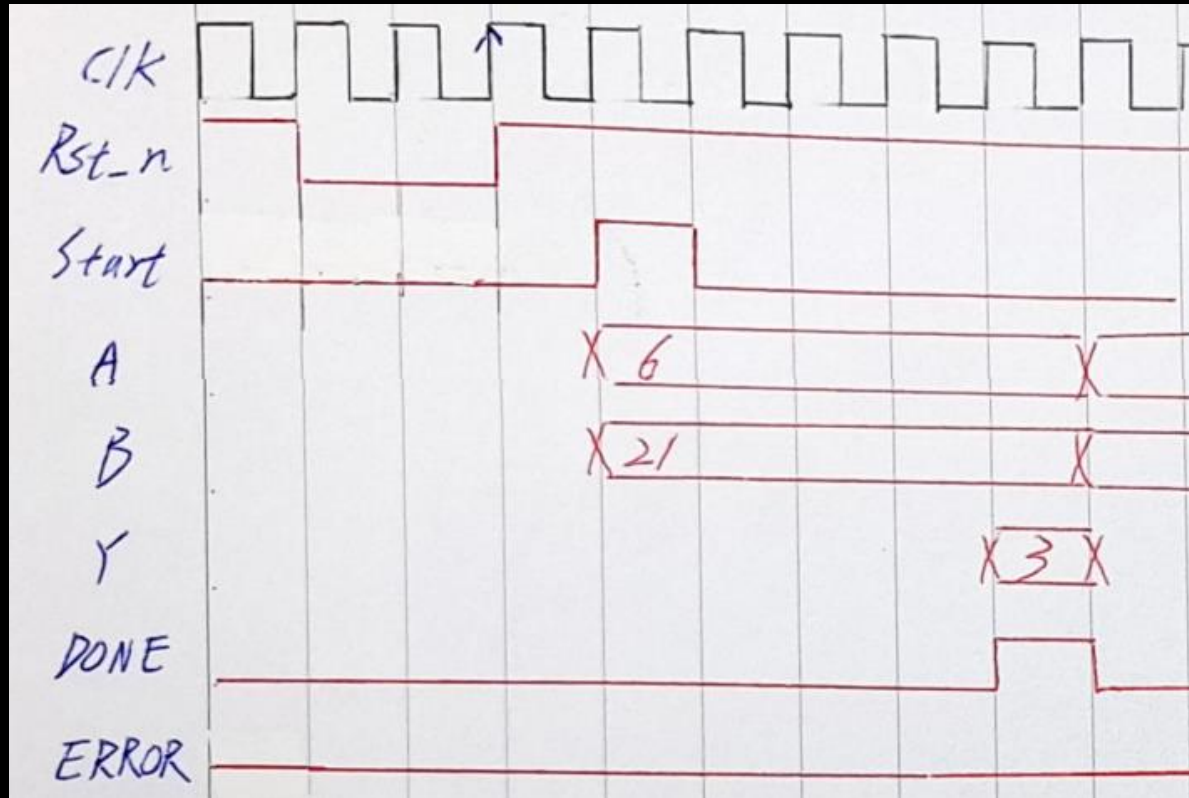




# Timing diagram (error case)

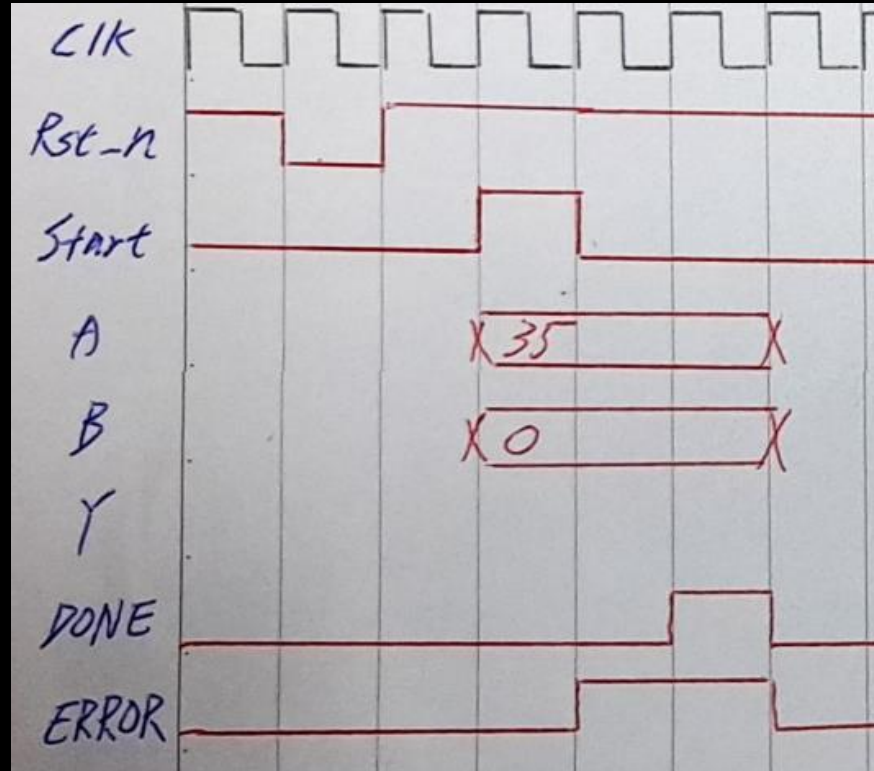


# nWave

- ❑ You can use waveform viewer to debug.
- ❑ Command
  - \$ncverilog tb.v design.v +access+r
  - \$nWave


# Open your waveform file

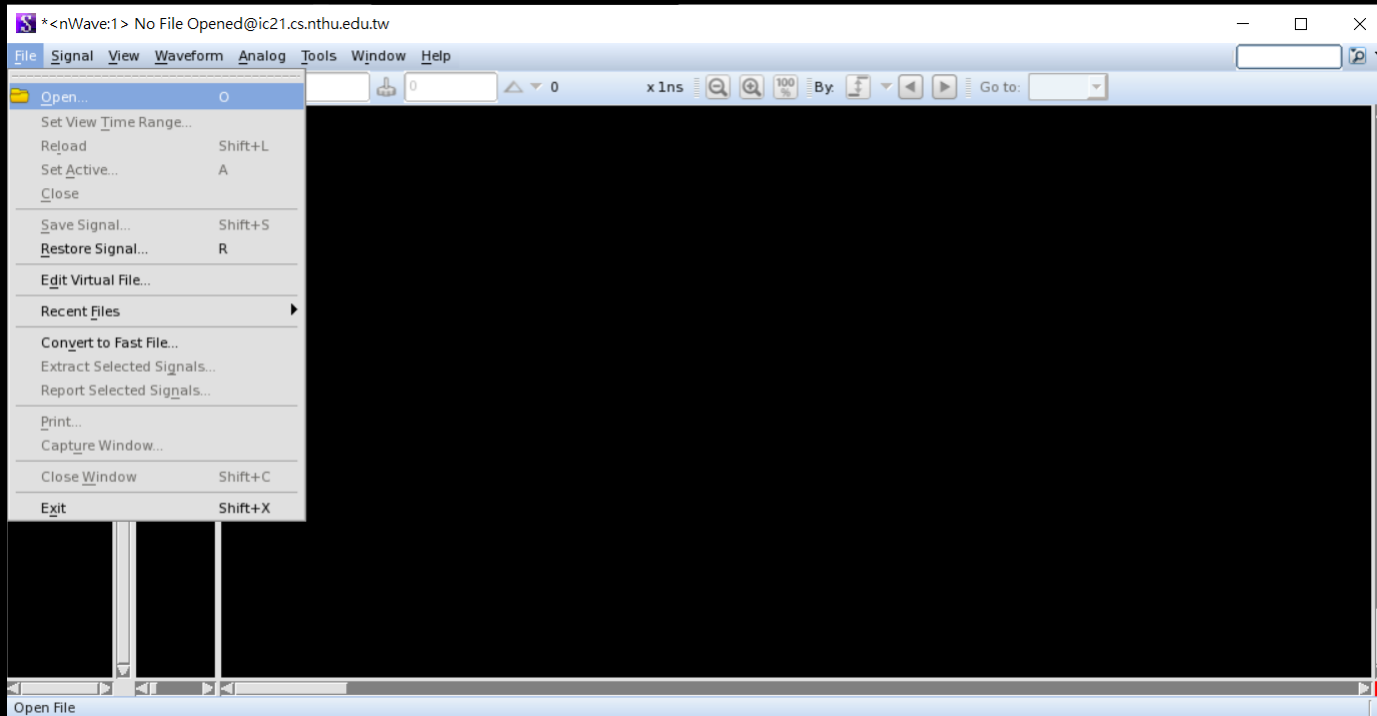


# Open your waveform file

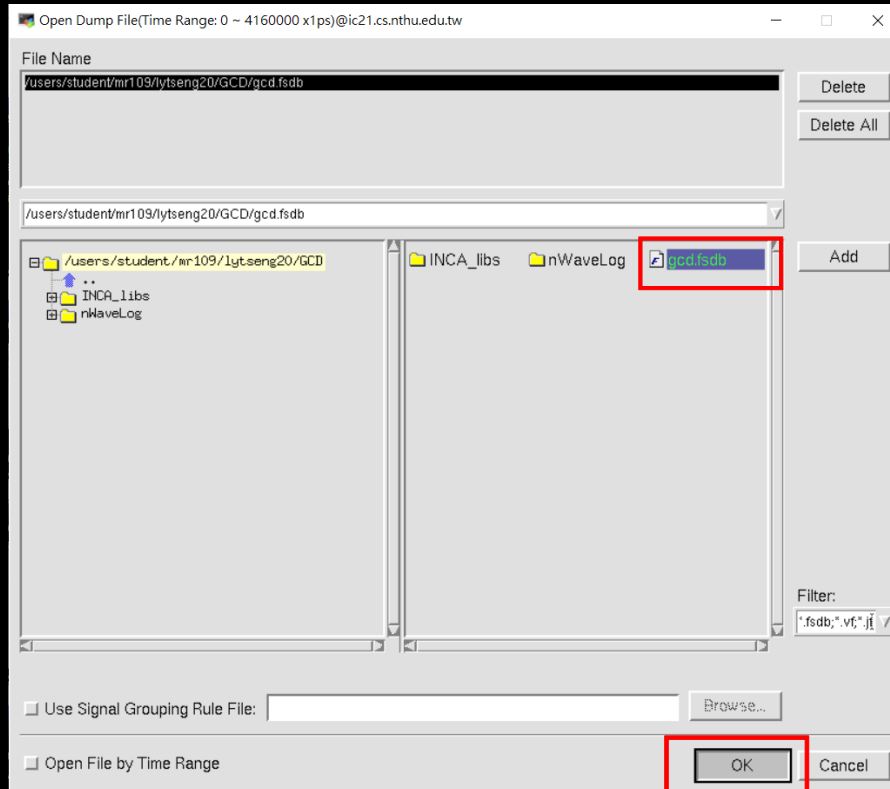

# Select signals you want to check

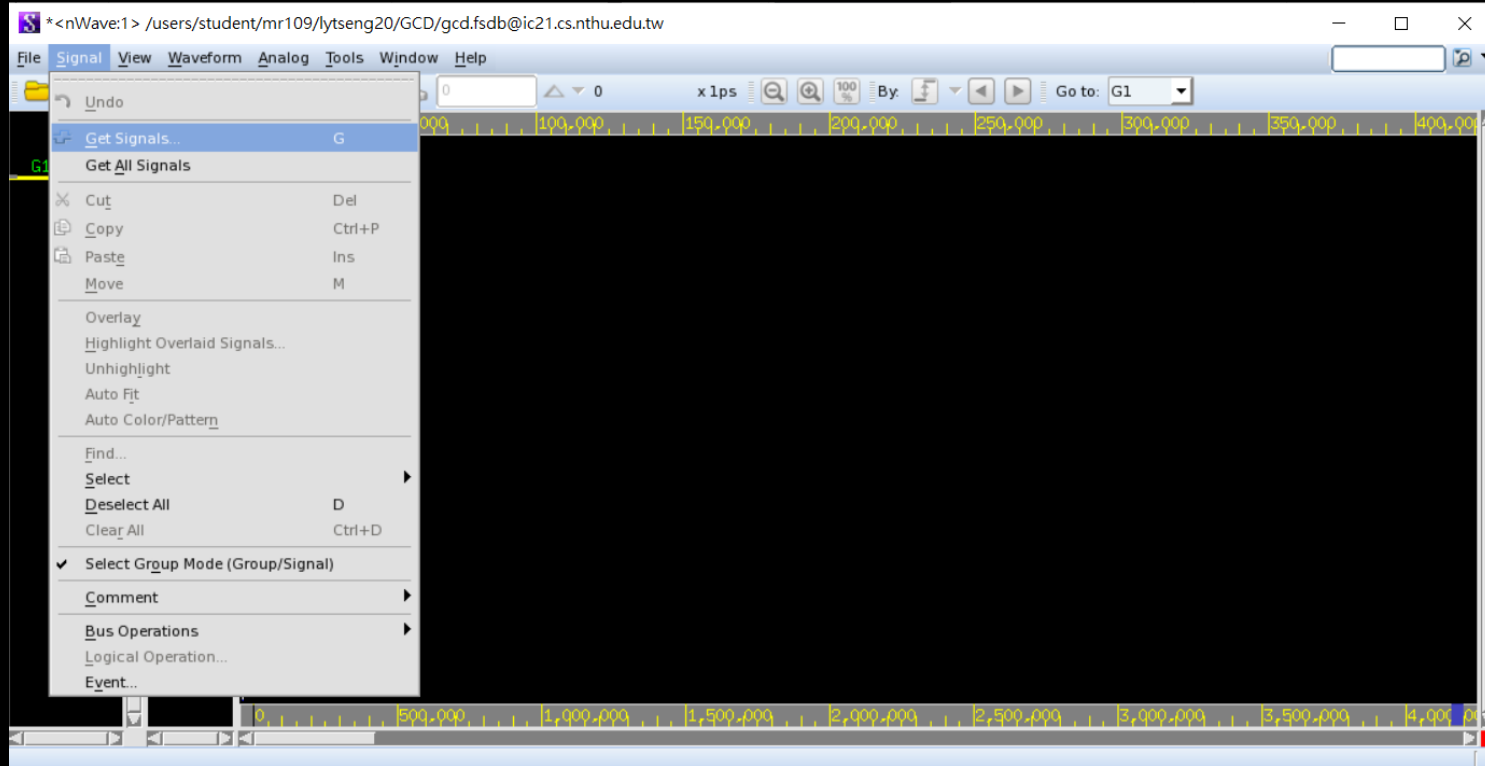


# Select signals you want to check

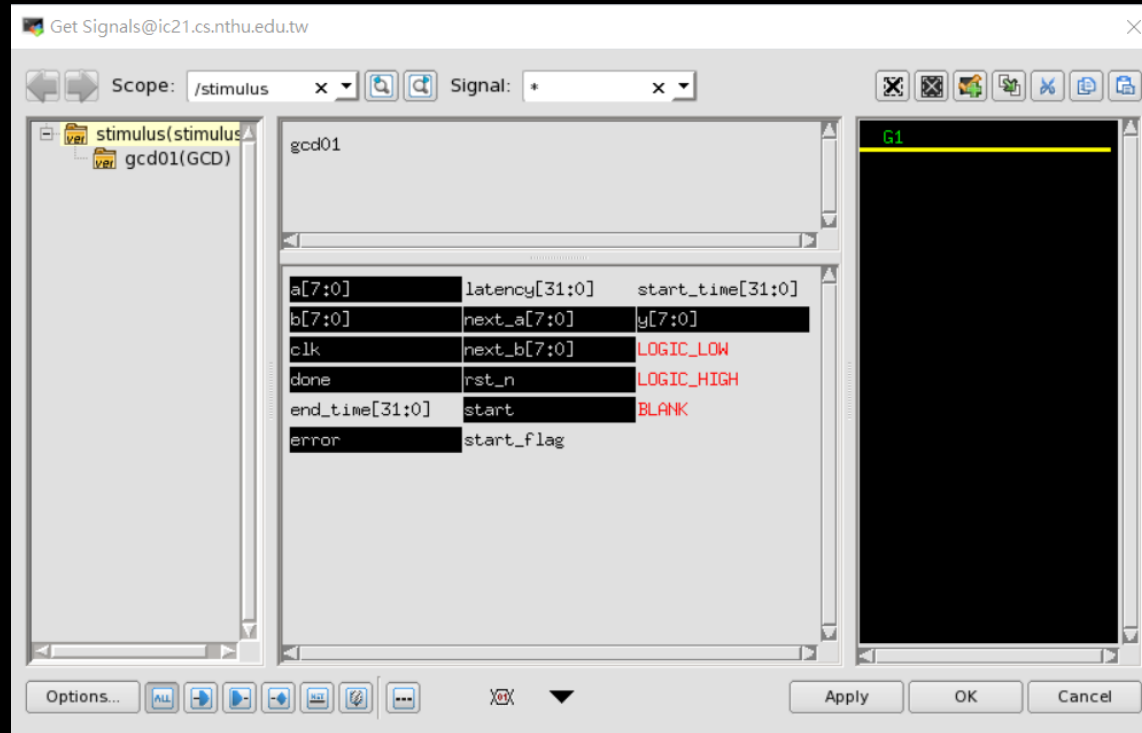

# Change signal value radix

? Example: next\_a (Hex->Dec)

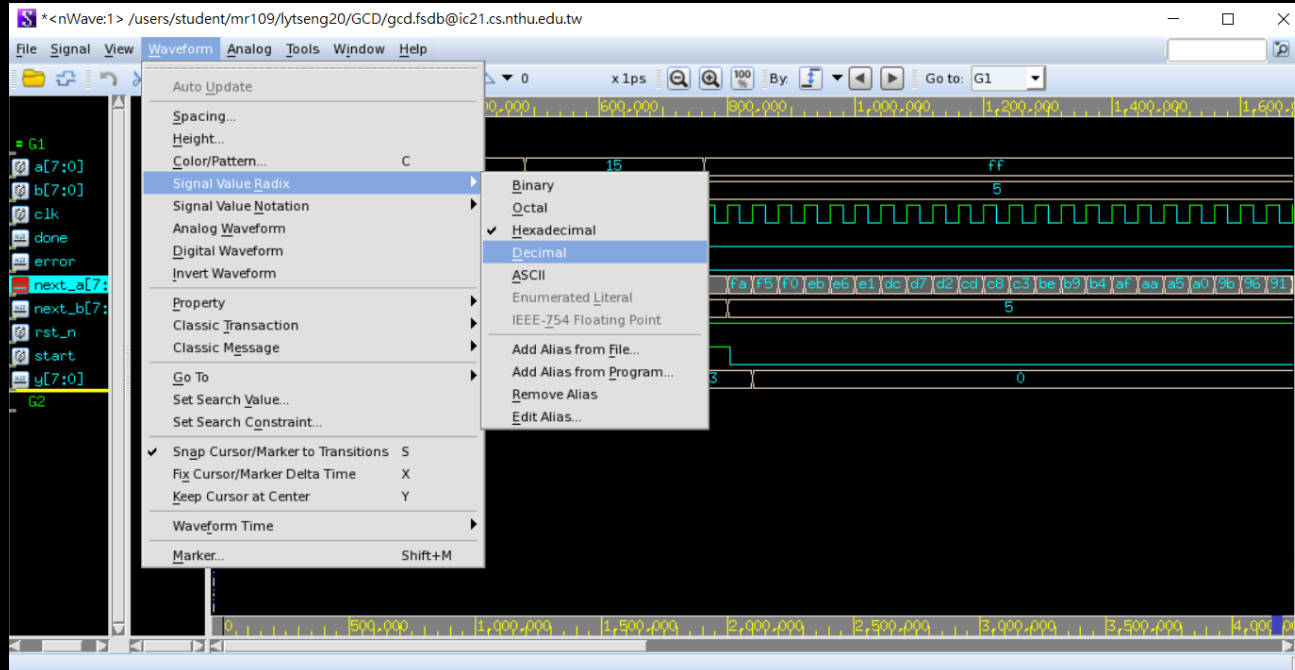

# Change signal value radix

Before



After





# Vim (text editor)

## ❓ Command

- `vim your_file.v`
- Press `i` to enter insert mode
  - ❓ You can edit your file in insert mode
  - ❓ Press `Esc` to leave insert mode
- type `:wq` to exit vim



```
1 module GCD (  
2     input wire CLK,  
3     input wire RST_N,  
4     input wire [7:0] A,  
5     input wire [7:0] B,  
6     input wire START,  
7     output reg [7:0] Y,  
8     output reg DONE,  
9     output reg ERROR  
10 );  
11  
12 wire found, err;  
13 reg [7:0] reg_a, reg_b, next_a, next_b;  
14 reg [7:0] big_one;  
15 reg error_next;  
16 reg [1:0] state, state_next;  
17  
18 parameter [1:0] IDLE = 2'b00;  
19 parameter [1:0] CALC = 2'b01;  
20 parameter [1:0] FINISH = 2'b10;  
21  
22  
23 endmodule
```



# Outline

- Function Description
- Framework Introduction in Block Diagram
- Testbench template
- nWave
- Precautions and Timeline



# Grading

- 60%: basic test cases (5)
- 40%: hidden test cases



# Warning

- Be careful of handling boundary conditions and make sure your testbench check for that
- For simplicity, use only subtraction for GCD calculation
- Use waveform viewer nWave to debug your timing issue
- Plagiarism is forbidden and gets you 0 point
  - Also punished by NTHUCS(drop out etc.)
- Discussion is pleasant, but no coding detail.



# Submission rule

- ❓ Lab 2 code submission due date & time:  
2021/05/27,23:59pm
- ❓ Please submit your Verilog codes to ILMS  
Lab2\_YourStudentID\_Codes.v

名稱	修改日期	類型	大小
 Lab2_YourStudentID_Codes.v	2021/5/1 下午 12:18	V 檔案	3 KB

- ❓ **\*Important\***: If you want to email us, please sent it to  
this email address [bibi1483070@gmail.com](mailto:bibi1483070@gmail.com)

